

(c) A cell of e.m.f. E and internal resistance r is connected to the circuit, as shown in Fig. 6.2.

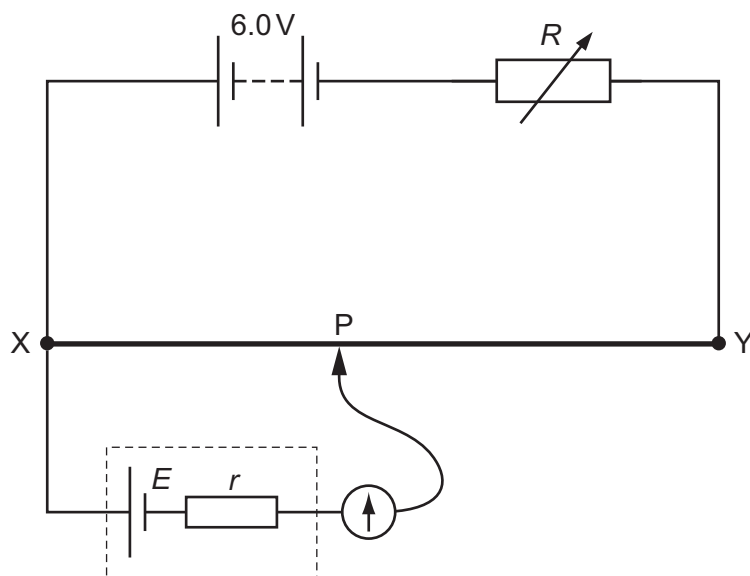


Fig. 6.2

Resistance R is unchanged.

The movable connection P is positioned on wire XY so that the galvanometer reading is zero. Distance XP is 1.24 m.

(i) Calculate E .

$$E = \dots\dots\dots \text{ V [2]}$$

(ii) The value of R is now decreased.

State and explain the change that must be made to the position of P on wire XY so that the galvanometer reads zero again.

.....

 [2]

[Total: 8]

