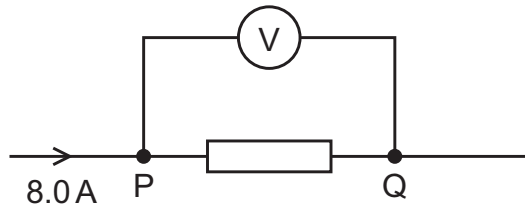


- 27** The diagram shows part of an electric circuit. The reading on the voltmeter is 16 V. The current in the resistor is 8.0 A.



One coulomb of charge flows from P to Q through the resistor.

How much energy is transferred in the resistor?

- A** 2.0 J **B** 8.0 J **C** 16 J **D** 128 J