

28 What is the combined resistance of a $3.0\ \Omega$ resistor and a $6.0\ \Omega$ resistor connected in parallel?

A $2.0\ \Omega$

B $4.5\ \Omega$

C $9.0\ \Omega$

D $18\ \Omega$