

29 A $5.0\ \Omega$ resistor is connected in series with a $10\ \Omega$ resistor.

There is a constant current in the $5.0\ \Omega$ resistor.

Which statement about the two resistors is correct?

- A** The current is greater in the $5.0\ \Omega$ resistor.
- B** The current is greater in the $10\ \Omega$ resistor.
- C** The potential difference (p.d.) is greater across the $5.0\ \Omega$ resistor.
- D** The potential difference (p.d.) is greater across the $10\ \Omega$ resistor.