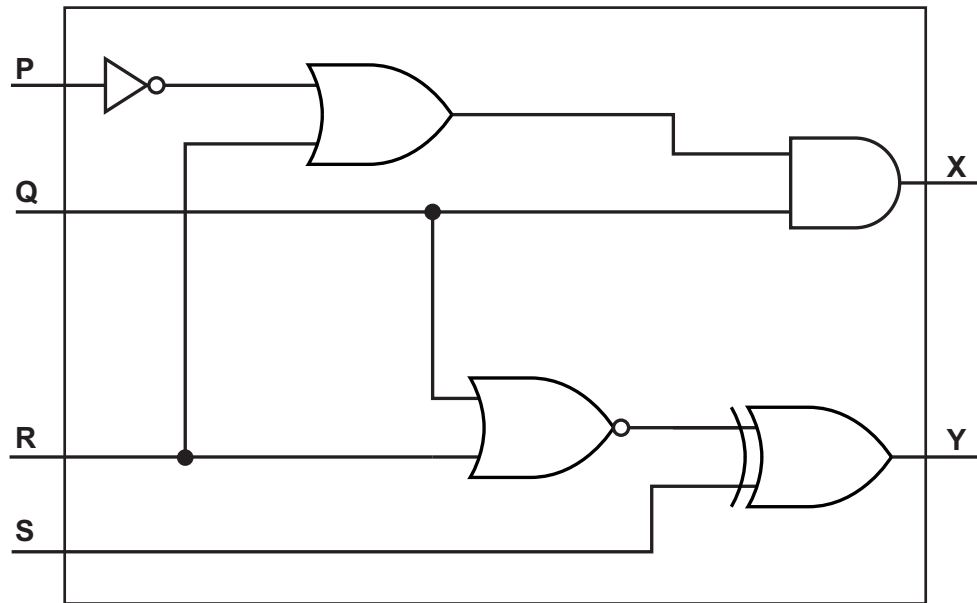




- 1 (a) Write the logic expressions for the following logic circuit.



X =

Y =

[2]

