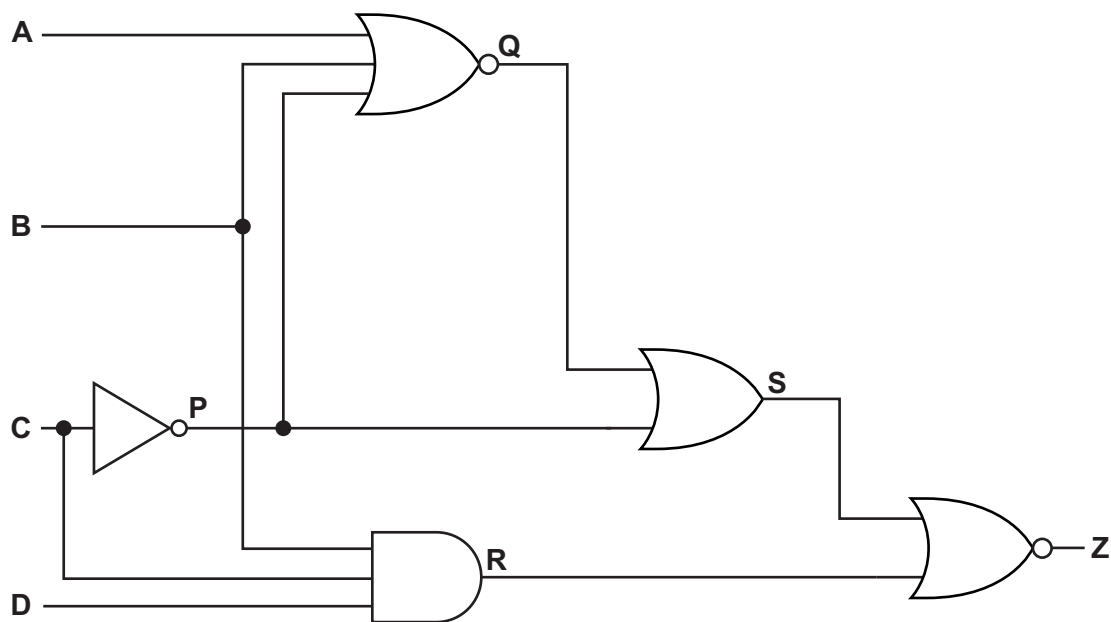




7 The diagram shows a logic circuit.



- (a) Complete the truth table for the given logic circuit.
Show your working.

				Working space				
A	B	C	D	P	Q	R	S	Z
0	0	0	0					
0	0	0	1					
0	0	1	0					
0	0	1	1					
0	1	0	0					
0	1	0	1					
0	1	1	0					
0	1	1	1					
1	0	0	0					
1	0	0	1					
1	0	1	0					
1	0	1	1					
1	1	0	0					
1	1	0	1					
1	1	1	0					
1	1	1	1					

