

3 This truth table represents a logic circuit.

INPUT				OUTPUT
A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

(a) Write the Boolean logic expression that corresponds to the given truth table as the sum-of-products.

Z =
..... [2]

(b) (i) Complete the Karnaugh map (K-map) for the given truth table.

AB					
CD		00	01	11	10
	00				
	01				
	11				
	10				

[2]

(ii) Draw loop(s) around appropriate group(s) in the K-map to produce an optimal sum-of-products. [2]

(iii) Write the Boolean logic expression from your answer to part (b)(ii) as the simplified sum-of-products.

Z =
..... [2]