



7 The truth table for a logic circuit is shown.

INPUT				OUTPUT
A	B	C	D	T
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

- (a) Write the Boolean logic expression that corresponds to the given truth table as the sum-of-products.

T =

..... [3]

