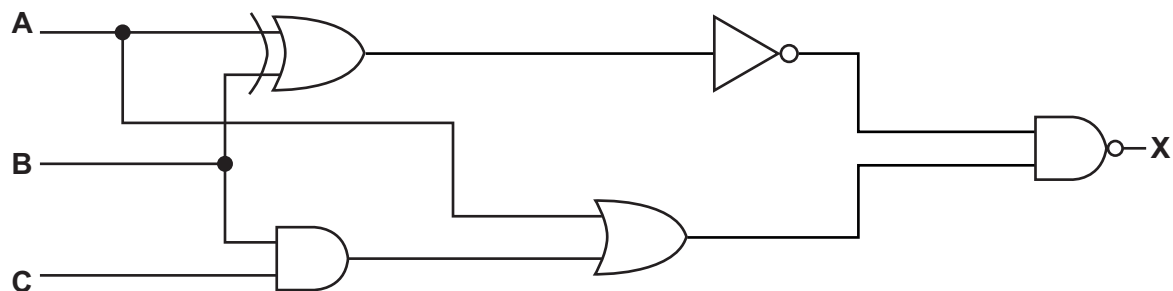


9 (a) Consider the following logic circuit:



Write the logic expression for the logic circuit. Do **not** simplify the expression.

$X =$ [2]

(b) Consider the following logic expression:

$$X = \text{NOT } ((A \text{ NAND } B) \text{ XOR } (\text{NOT } A \text{ OR } \text{NOT } C))$$

A truth table for the logic expression is given:

Row number	A	B	C	X
1	0	0	0	1
2	0	0	1	0
3	0	1	0	1
4	0	1	1	0
5	1	0	0	1
6	1	0	1	0
7	1	1	0	1
8	1	1	1	1

There are **three** errors in the truth table.

Identify the **three** errors in the truth table by writing the row numbers with an incorrect output.

Error 1 Row number

Error 2 Row number

Error 3 Row number

[2]

