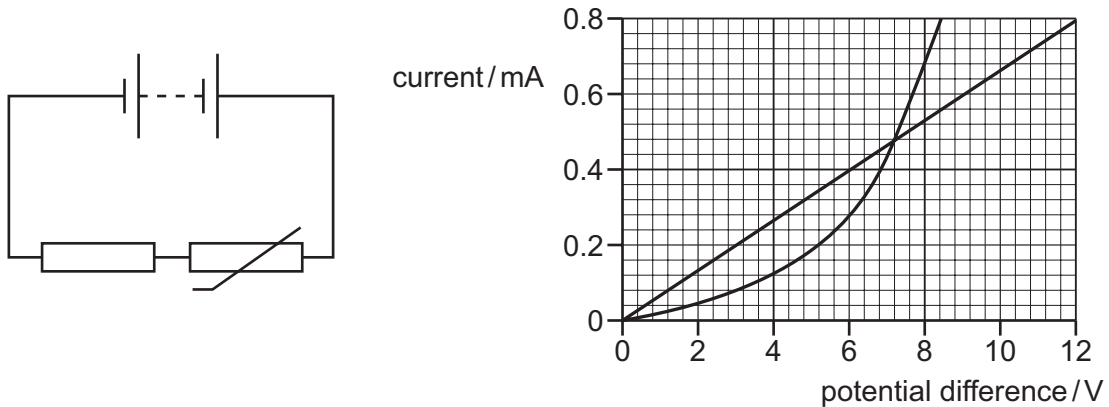


- 35 The diagram shows a circuit containing a thermistor, a fixed resistor and a battery.


The graph shows the  $I$ - $V$  characteristics of both components.



The battery has an e.m.f. of 12 V and negligible internal resistance.

What is the current in the fixed resistor?

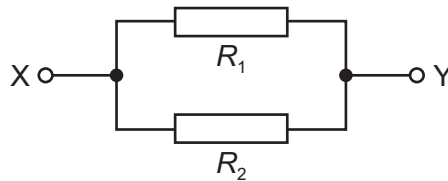- A 0.36 mA      B 0.40 mA      C 0.48 mA      D 0.80 mA
- 36 Two resistors of resistances  $R_1$  and  $R_2$  are connected in parallel.



What is the combined resistance between X and Y?

- A  $R_1 + R_2$       B  $\frac{R_1 R_2}{R_1 + R_2}$       C  $\frac{R_1 + R_2}{R_1 R_2}$       D  $\frac{R_1}{R_2}$