

- (b) Wire Y is identical to wire X. Wire Y is added to the circuit in parallel with wire X, as shown in Fig. 6.2.

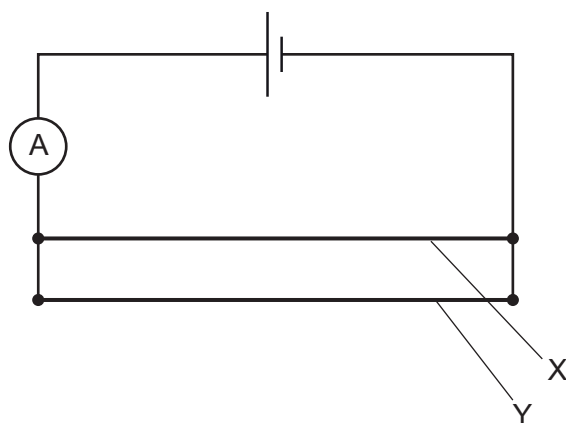


Fig. 6.2

State and explain the effect, if any, of this change on:

- (i) the reading on the ammeter

.....

 [2]

- (ii) the average drift speed of the charge carriers in X.

.....
 [1]

[Total: 9]

