

- 6 (a) Define electric potential difference across a component.

.....
 [1]

- (b) A circuit contains four resistors and a battery of electromotive force (e.m.f.) 8.0 V with negligible internal resistance. When the variable resistor has resistance R , the currents in the circuit are 0.030 A , I_1 and I_2 , as shown in Fig. 6.1.

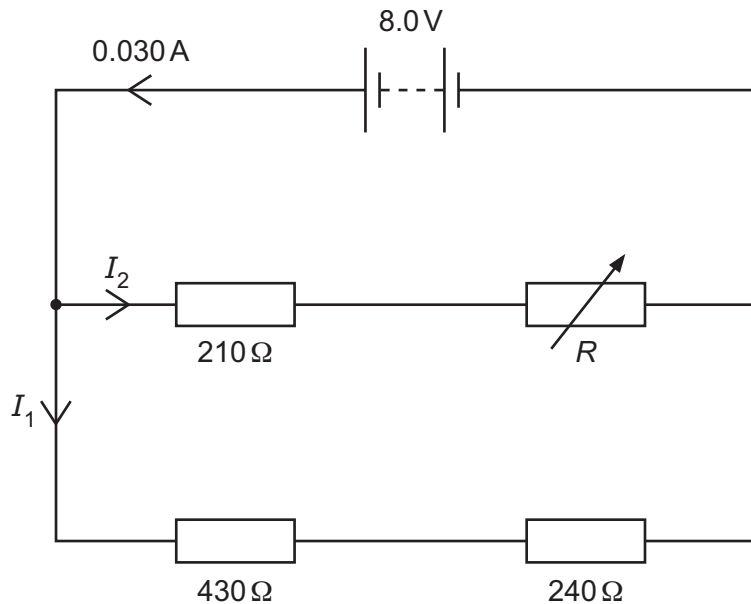


Fig. 6.1

- (i) Determine the charge passing through the battery in a time of 4.0 minutes.

charge = C [2]

- (ii) Calculate I_1 .

I_1 = A [2]

