



(iii) Calculate I_2 .

$I_2 = \dots\dots\dots$ A [1]

(iv) Determine R .

$R = \dots\dots\dots$ Ω [2]

