

- 6 Fig. 6.1 shows a circuit that rectifies an alternating input voltage V_{IN} and produces an output voltage V_{OUT} across a resistor R .

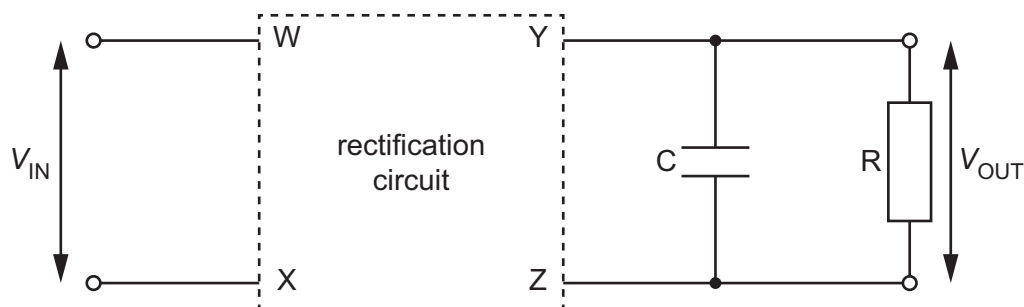


Fig. 6.1

The four terminals of the rectification circuit are labelled W, X, Y and Z.
A capacitor C is connected in parallel with resistor R .

- (a) (i) State what is meant by rectification.

.....
..... [1]

- (ii) State the purpose of capacitor C .

.....
..... [1]

- (b) Fig. 6.2 shows the variations with time t of the potential differences (p.d.s) V_{IN} and V_{OUT} .

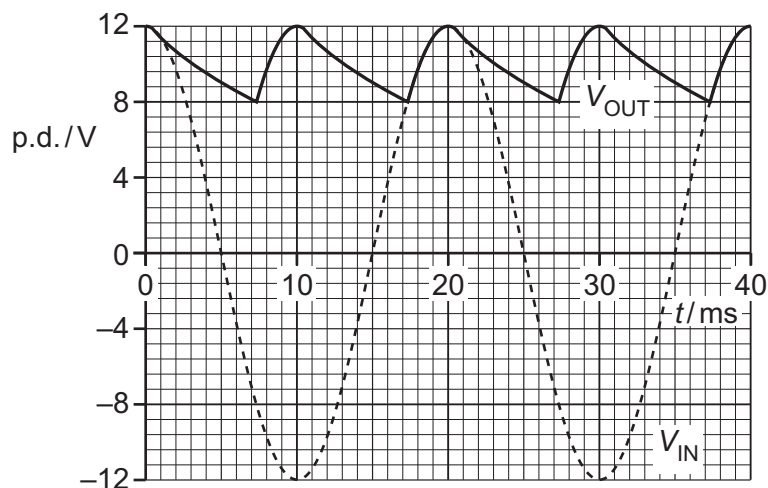


Fig. 6.2

