



(ii) the resistance R , in $\text{k}\Omega$

$R = \dots\dots\dots \text{k}\Omega$ [2]

(iii) the time constant τ of the circuit.

$\tau = \dots\dots\dots \text{s}$ [2]

(c) Use Fig. 7.2, Fig. 7.3 and your answer in (a) to explain why the variation of Q with t is exponential in nature.

.....

.....

.....

.....

..... [3]

[Total: 10]

