

8 Fig. 8.1 shows a circuit that produces rectification of an alternating input voltage.

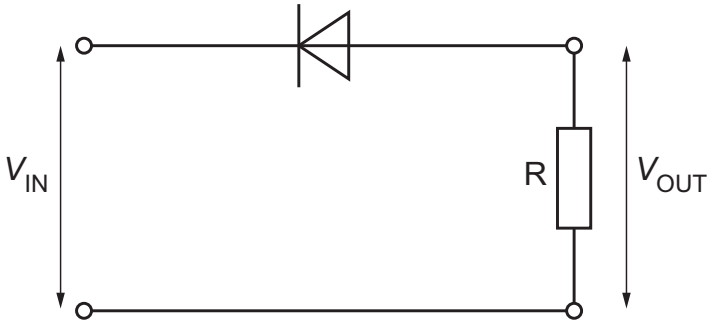


Fig. 8.1

The input voltage V_{IN} is sinusoidal. The rectified output voltage V_{OUT} is applied across resistor R. The variation of V_{IN} with time t has amplitude V_0 and period T , as shown in Fig. 8.2.

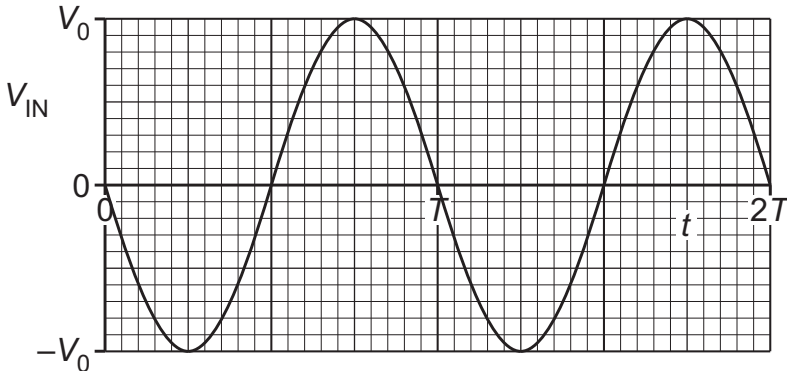


Fig. 8.2

The root-mean-square (r.m.s.) value of V_{IN} is 6.0 V.

- (a) (i) State the type of rectification produced by the circuit of Fig. 8.1.
- [1]
- (ii) Calculate V_0 .

$V_0 =$ V [1]

(b) Resistor R has resistance 45 Ω.

Assume that there is no p.d. across the diode when it is conducting.

- (i) Determine the peak power P_0 in the resistor.

$P_0 =$ W [2]

- (ii) On Fig. 8.3, sketch the variation of the power P in the resistor with t between $t = 0$ and $t = 2T$.

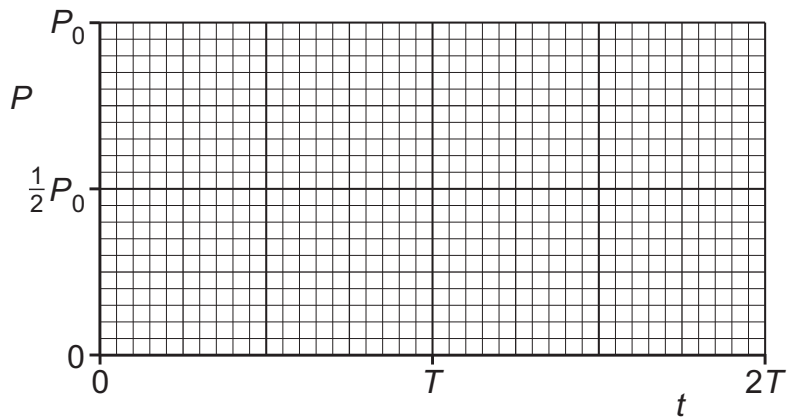


Fig. 8.3

[3]

- (iii) Use the answer in (b)(ii) to explain why the mean power in the resistor is $\frac{1}{4}P_0$.
-
-
- [2]

- (iv) Use the information in (b)(iii) to determine the r.m.s. value of V_{OUT} .

r.m.s. voltage = V [1]