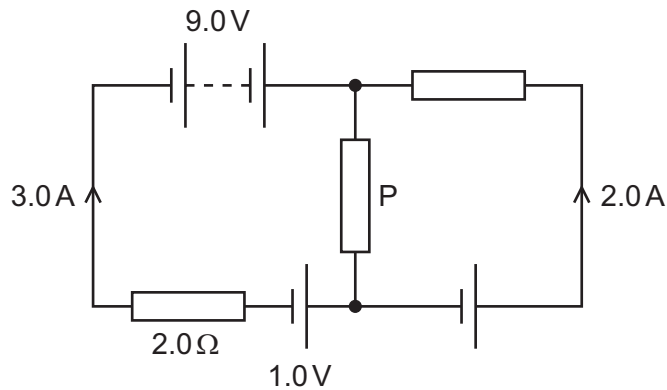
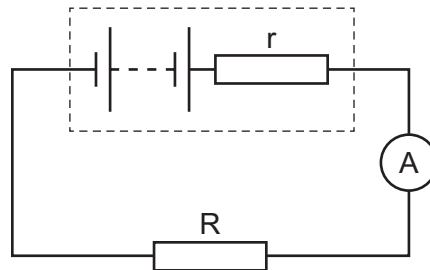


- 34** The diagram shows a circuit containing a battery and cells with negligible internal resistance. Some values of current, electromotive force (e.m.f.) and resistance are shown. One resistor is labelled P.



What is the resistance of resistor P?

- A** 0.40Ω **B** 0.80Ω **C** 2.0Ω **D** 2.8Ω
- 35** The diagram shows a circuit with a battery connected to a resistor R. The battery has an internal resistance represented by resistor r.



A second resistor, identical to R, is connected in parallel with R.

Which row describes the changes to the potential difference (p.d.) across r and the current shown on the ammeter when the second resistor is connected?

	p.d. across r	current shown on ammeter
A	decreases	decreases
B	decreases	increases
C	increases	decreases
D	increases	increases