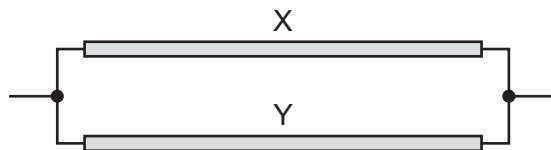


- 36 Two identical wires X and Y, each of length L and radius r , are connected in parallel as shown.



The total resistance of this combination is R_1 .


Wire X is replaced with a wire of the same material with length L and radius $2r$.

The total resistance of the new combination is R_2 .

What is the ratio $\frac{R_1}{R_2}$?

- A $\frac{2}{5}$ B $\frac{2}{3}$ C $\frac{3}{2}$ D $\frac{5}{2}$

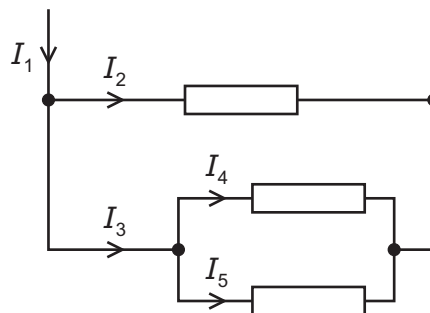- 37 The diagram shows the currents in part of an electric circuit.




The resistors are identical.

Which equation is **not** correct?

- A $I_1 = I_2 + I_4 + I_5$
 B $I_2 = I_1 - I_3$
 C $I_2 = I_3 + I_4 + I_5$
 D $I_4 = I_3 - I_5$

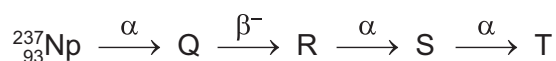- 38 The diagram shows a sequence of radioactive decays involving three α -particles and a β^- particle.



What is nuclide T?

- A ${}_{88}^{225}\text{Ra}$ B ${}_{88}^{231}\text{Ra}$ C ${}_{90}^{225}\text{Th}$ D ${}_{90}^{229}\text{Th}$