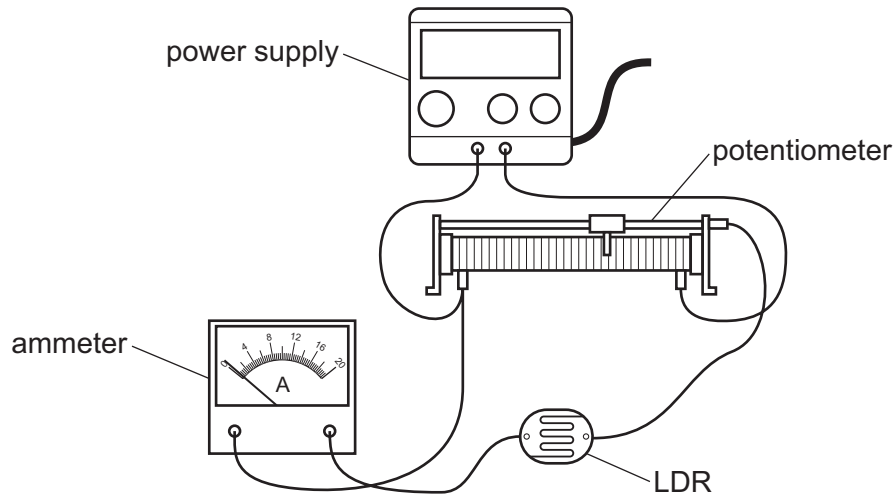
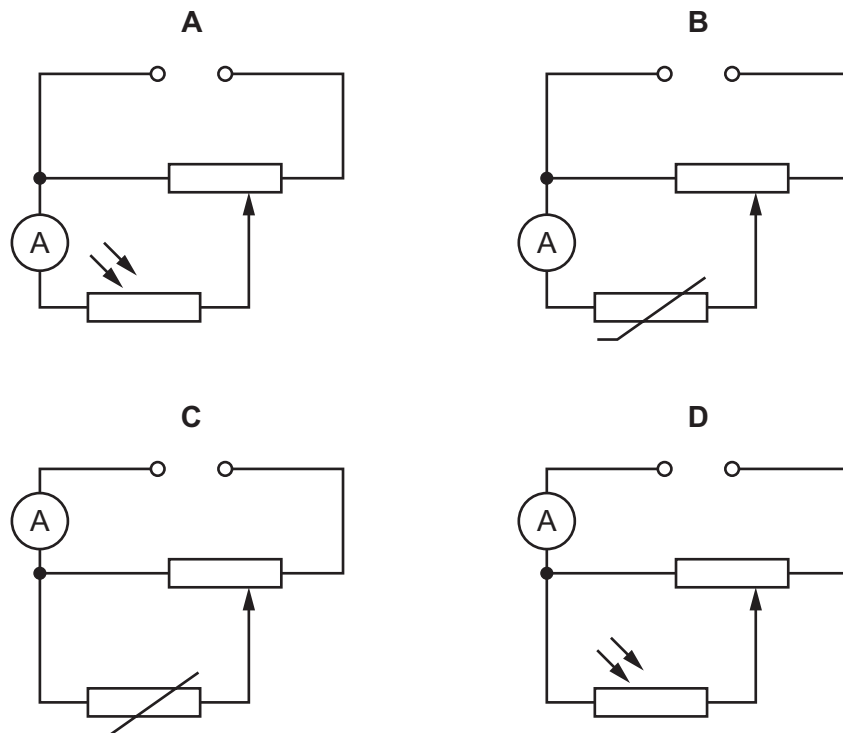


- 33 The diagram shows an electrical circuit containing a light-dependent resistor (LDR).



What is the circuit diagram for this circuit?



- 34 A copper wire of length 2 m has a circular cross-section. There is a constant current in the wire when it is connected to a mobile phone in order to charge the battery.

The wire has a fault. A 1 m length of the wire has half the diameter of the other 1 m length.

The power dissipated in the thicker length of wire is P .

What is the power dissipated in the thinner length of wire?

- A $\frac{1}{4}P$ B $\frac{1}{2}P$ C $2P$ D $4P$