


- 35** A wire carries a current of 5.6 A.

What is the number of conduction electrons that pass a point on the wire in a time of 20 s?

- A** 1.8×10^{18} **B** 2.2×10^{19} **C** 3.5×10^{19} **D** 7.0×10^{20}

- 36** Four resistors of resistance R , $2R$, $3R$ and $4R$ are connected to form a network.

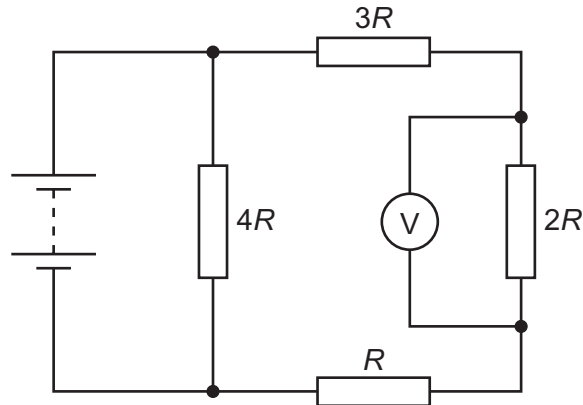A battery of negligible internal resistance and a voltmeter are connected to the resistor network as shown.



The voltmeter reading is 2 V.

What is the electromotive force (e.m.f.) of the battery?

- A** 2 V **B** 4 V **C** 6 V **D** 10 V