

You may not need to use all of the materials provided.

- 2** In this experiment, you will investigate the resistance of a light-dependent resistor (LDR) using the light from a light-emitting diode (LED).

(a) (i) • Using the LED, set up the circuit shown in Fig. 2.1.

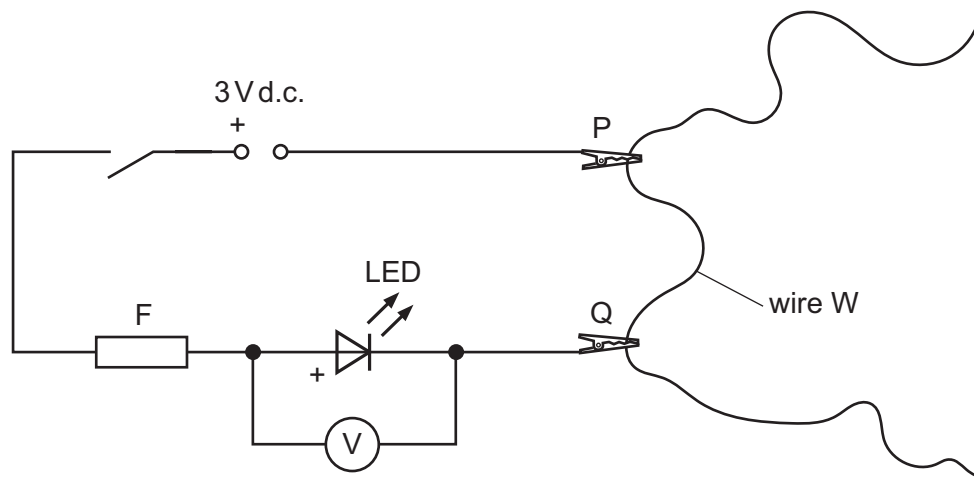


Fig. 2.1

- Ensure that the positive terminal of the power supply and the positive terminal of the LED are connected as shown in Fig. 2.1.
- P and Q are crocodile clips. Position P and Q so that there is approximately 10 cm of wire W between P and Q.
- Close the switch. The LED should light.
- Open the switch.
- Using the LDR and ohmmeter, set up a second circuit as shown in Fig. 2.2.

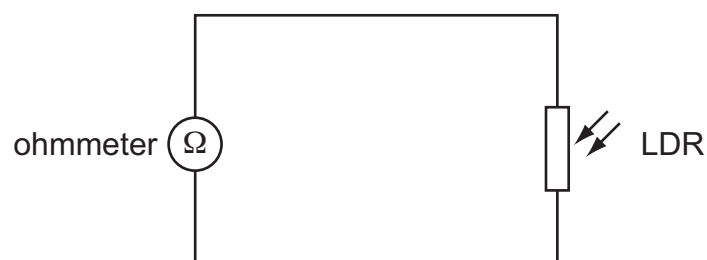


Fig. 2.2

