

- 6 Fig. 6.1 shows part of a bridge rectifier circuit that can be used for rectification of an alternating input voltage V_{IN} .

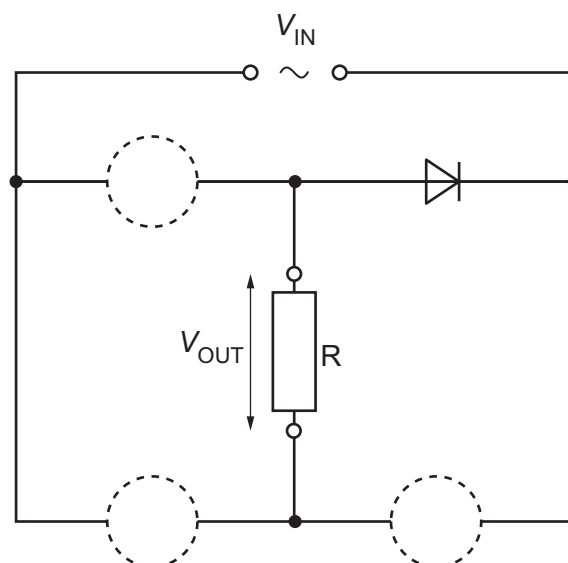


Fig. 6.1

The circuit contains four diodes, one of which is shown.
The rectified output voltage V_{OUT} is applied across load resistor R .

- (a) (i) State what is meant by rectification.

.....
..... [1]

- (ii) State the name of the type of rectification produced by a bridge rectifier circuit.

..... [1]

- (iii) Complete the circuit in Fig. 6.1 by drawing the three missing diodes inside the dashed circles. [2]

