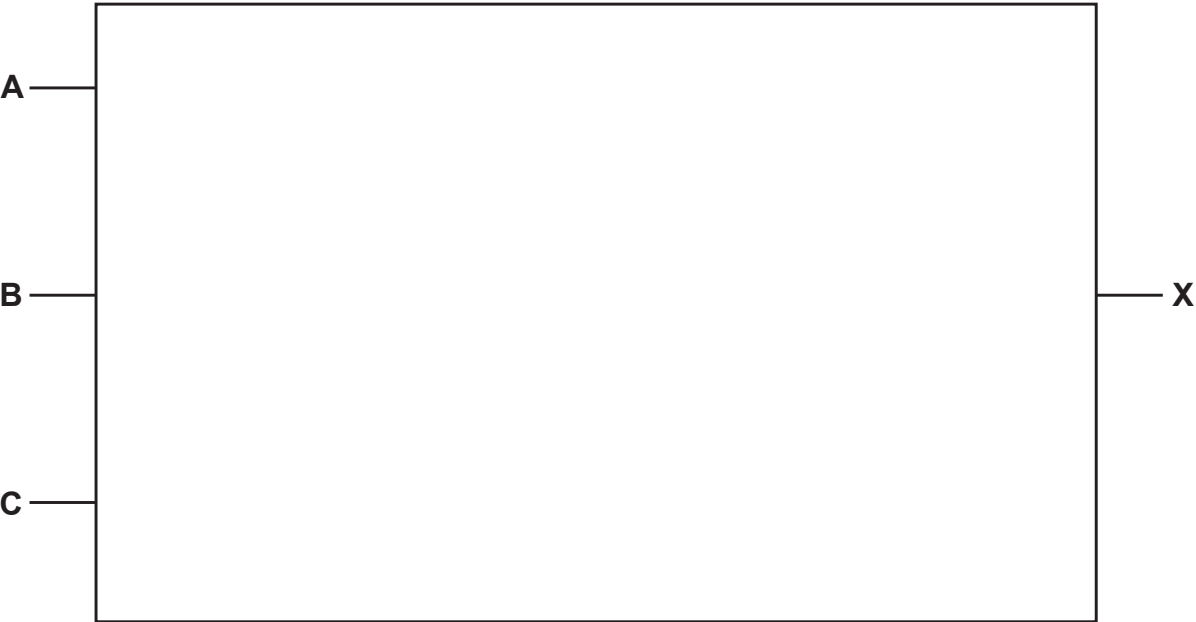


7 Consider the logic expression:

$$X = (A \text{ XOR } B) \text{ AND } (\text{NOT } B \text{ AND } C)$$

(a) Draw a logic circuit for this logic expression. Each logic gate must have a maximum of **two** inputs. Do **not** simplify this logic expression.



[4]

(b) Complete the truth table from the given logic expression.

A	B	C	Working space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[4]