
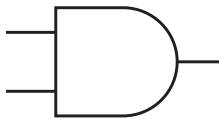
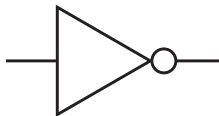
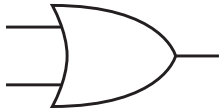


2 (a) Four logic gate symbols and five logic functions are shown.

Draw one line to link each logic gate symbol to the appropriate logic function.

Not all logic functions will be used.

Logic gate symbol

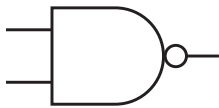

Logic function

AND

XOR


NOT

NAND

OR

[4]

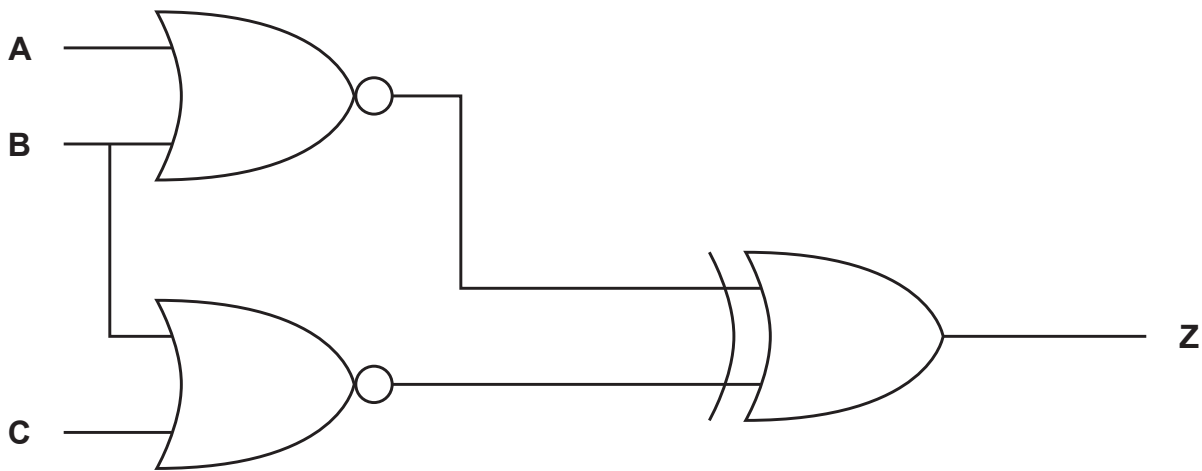(b) Complete the truth table for this logic circuit.



A	B	C	Working space	Z
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[4]