



- 8 (a) Draw the symbol for an XOR logic gate **and** complete the truth table for it.

XOR logic gate symbol:



Truth table:

A	B	X
0	0	
0	1	
1	0	
1	1	

[2]

