 


- 7 (a) Draw the symbol for a NOR logic gate and complete the truth table for it.

NOR logic gate symbol:



Truth table:

A	B	Z
0	0	
0	1	
1	0	
1	1	

[2]

- (b) Consider the rules given in the following table:

Input	Binary value	Description
L	0	dark
	1	light
M	0	no motion detected
	1	motion detected
S	0	no sound detected
	1	sound detected

A security system uses sensors to sound an alarm if an intruder is detected.

The alarm sounding is represented by the output **A = 1**.

The alarm sounds if it is dark and if either motion or sound or both motion and sound are detected.

