



(i) Write the logic expression for the security system.

A =

..... [2]

(ii) Complete the truth table for the security system.

L	M	S	Working space	A
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[4]

