


9 Consider the logic expression:

$$X = (\text{NOT } P \text{ OR } Q) \text{ NAND } (Q \text{ XOR } R)$$

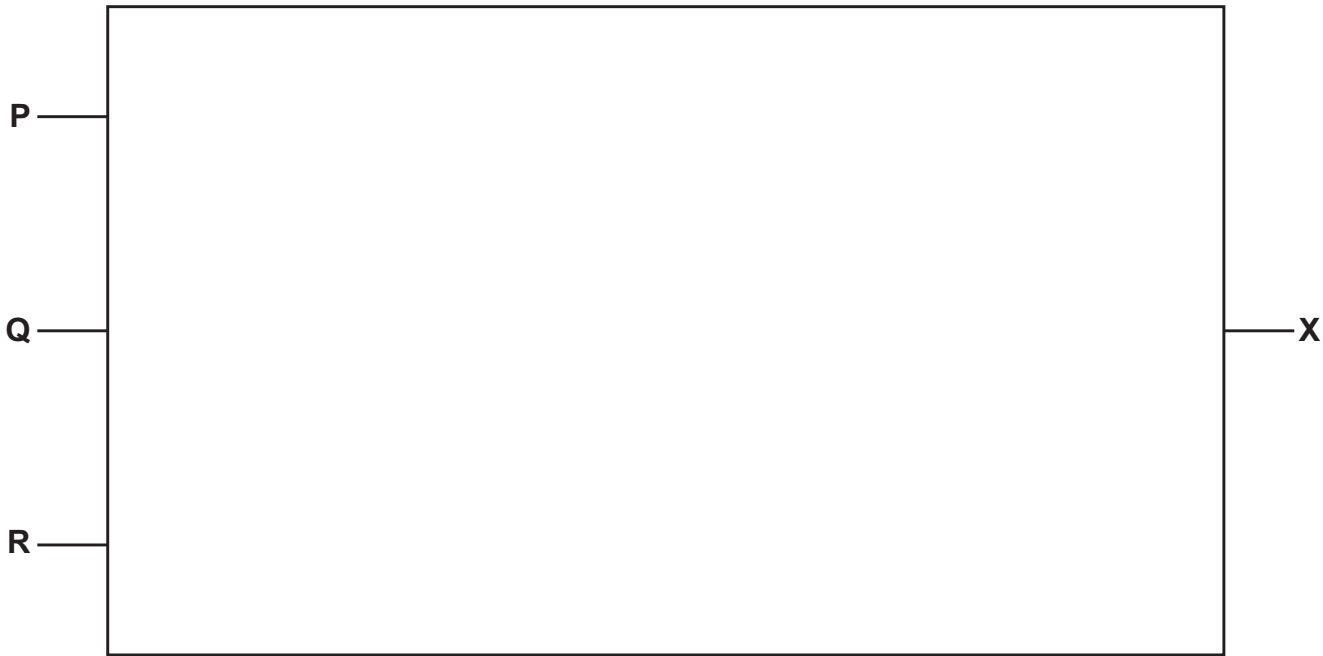(a) Draw a logic circuit for this logic expression.

Each logic gate must have a maximum of **two** inputs.

Do **not** simplify the logic expression.



[4]

(b) Complete the truth table for the given logic expression.

P	Q	R	Working space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[4]