



- 8 A logic circuit is to be built to control the automatic opening of a window. The window **W** opens if the temperature **T** is too high, the heater **H** is off, and the air conditioning **A** is off.

air conditioning A	air conditioning off	0
	air conditioning on	1
temperature T	not too high	0
	too high	1
heater H	heater off	0
	heater on	1
window W	window closed	0
	window open	1

Complete the truth table for this problem.

A	T	H	W
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

[4]

