

30 Which statement explains where the switch for an electric lamp is connected?

- A** The switch is in **either** the live wire **or** in the neutral wire as both wires carry the current.
- B** The switch is in the earth wire to prevent the fuse from blowing when the lamp is in use.
- C** The switch is in the live wire so that the lamp is disconnected from the mains supply when the switch is off.
- D** The switch is in the neutral wire to prevent current leakage when the lamp is switched off.