

- 1 Tick (✓) **one** box to complete this sentence.

This flowchart symbol



A represents a subroutine.

☐

B represents a decision.

☐

C represents an input/output.

☐

D represents a terminator.

☐





[1]

- 2 (a) **Four** logic gate symbols and **five** logic functions are shown.

Draw **one** line to link each logic gate symbol to the appropriate logic function.

Not all logic functions will be used.

Logic gate symbol

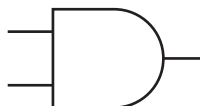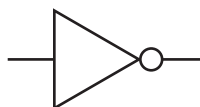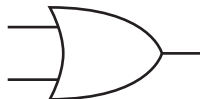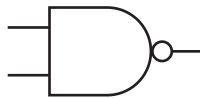

Logic function

AND

XOR

NOT

NAND

OR

[4]