



1 Tick (✓) **one** box to show which of the following is used to validate data on input.

- | | | |
|---|--------------------|--------------------------|
| A | checksum | ☐ |
| B | double entry check | ☐ |
| C | type check | ☐ |
| D | visual check | ☐ |

[1]

2 Tick (✓) **one** box to show a method used to construct a solution to a problem.

- | | | |
|---|-------------------|--------------------------|
| A | abstraction | ☐ |
| B | structure diagram | ☐ |
| C | test data | ☐ |
| D | variable | ☐ |

[1]

3 **Four** logic gates and **five** logic gate symbols are shown.

Draw **one** line to link each logic gate to its correct symbol. **Not** all logic gate symbols will be used.

Logic gate






AND

NAND

NOR

XOR

Logic gate symbol

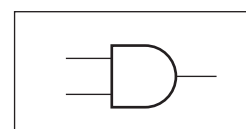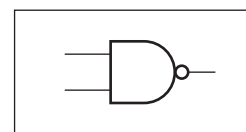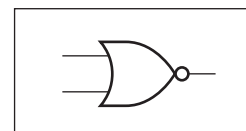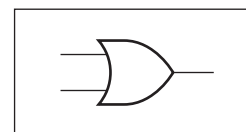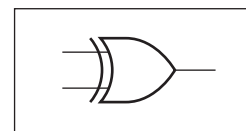

[4]

